

ECE 550: Fundamentals of Computer Systems and Engineering

Storage and Clocking

Admin

- Reading
 - Finish up Chapter 3
- Recitation
 - How is it going?
 - VHDL questions/issues?
- Homework
 - Homework 1
 - Submissions vis Sakai

VHDL: Behavioral vs Structural

- A few words about this
 - Structural:
 - Spell out at (roughly) gate level
 - Abstract piece into **entities** for abstraction/re-use
 - Very easy to understand what synthesis does to it
 - Behavioral:
 - Spell out at higher level
 - Sequential statements, for loops, process blocks
 - Can be difficult to understand how it synthesizes
 - Difficult to resolve performance issues

Last time...

- Who can remind us what we did last time?



So far...

- We can make logic to compute “math”
 - Add, subtract,... (we’ll see multiply/divide later)
 - Bitwise: AND, OR, NOT,...
 - Shifts
 - Selection (MUX)
 - ...pretty much anything
- But processors need state (hold value)
 - Registers
 - ...

Memory Elements

- All the circuits we looked at so far are **combinational circuits**: the output is a Boolean function of the inputs.
- We need circuits that can remember values. (registers)
- The output of the circuit is a function of the input AND a function of a stored value (state) .
- Circuits with memory are called **sequential circuits**.
- Key to storage: loops from outputs to inputs




NOR-based Set-Reset (SR) Latch

  




R	S	Q
0	0	Q
0	1	1
1	0	0
1	1	-

Don't set both S & R to 1




Set-Reset Latch (Continued)

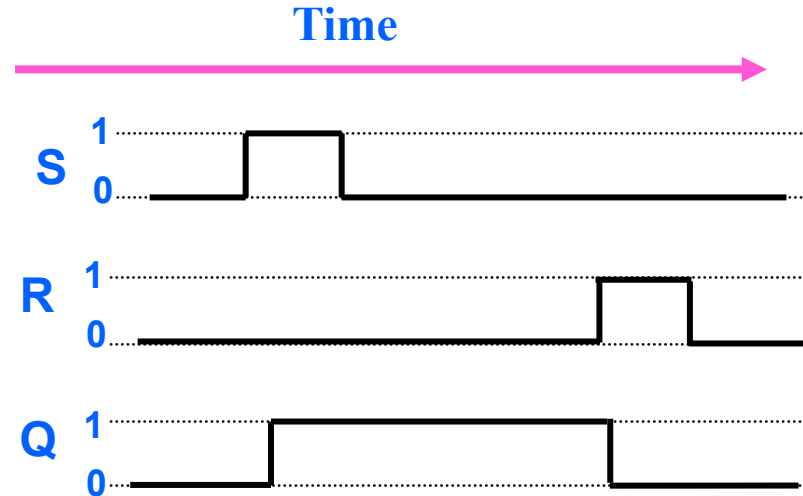  




Set-Reset Latch (Continued)

   

Set-Reset Latch (Continued)

   

Set-Reset Latch (Continued)

   


Until Reset Signal Goes High

Then Output Signal Goes Low

SR Latch


- Downside: S and R at once = chaos
- Downside: Bad interface
- So let's build on it to do better

Data Latch (D Latch)

 

We start with SR Latch

Data Latch (D Latch)

 


We start with SR Latch

**..and add some gates at the front
which change the interface**


Data + Enable

Data Latch (D Latch)

 


D	E	Q
0	1	0
1	1	1
-	0	Q


Time

 


Data Latch (D Latch)

 

D	E	Q
0	1	0
1	1	1
-	0	Q

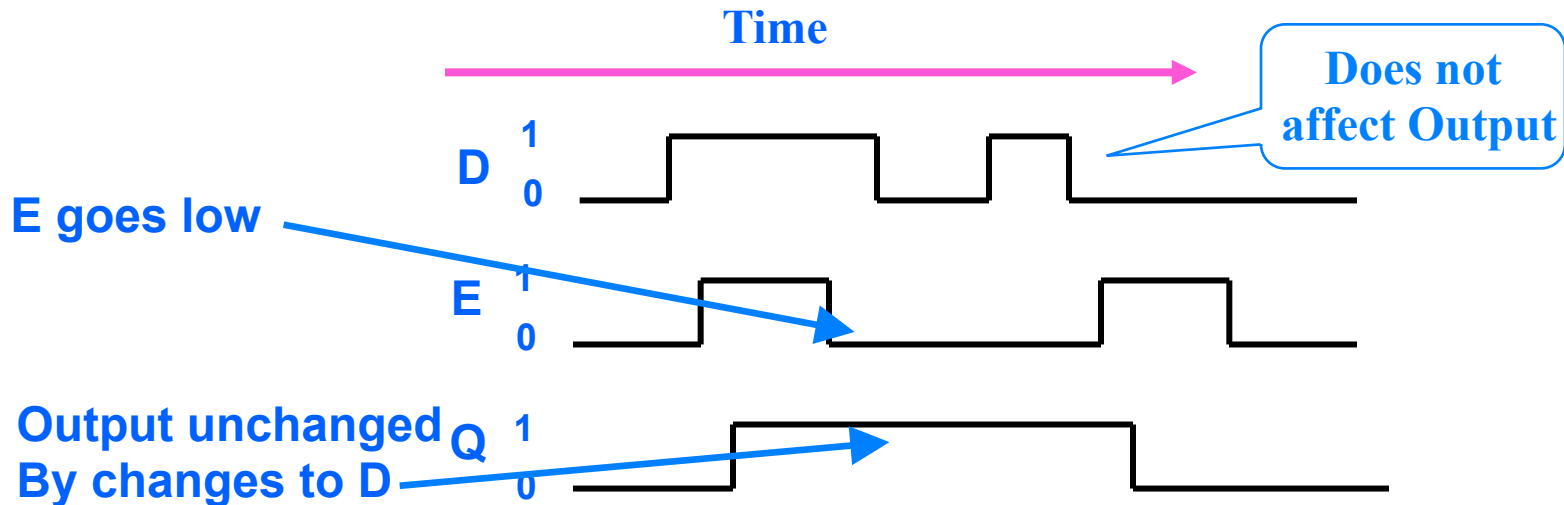


Data Latch (D Latch)

 


D	E	Q
0	1	0
1	1	1
-	0	Q


Time

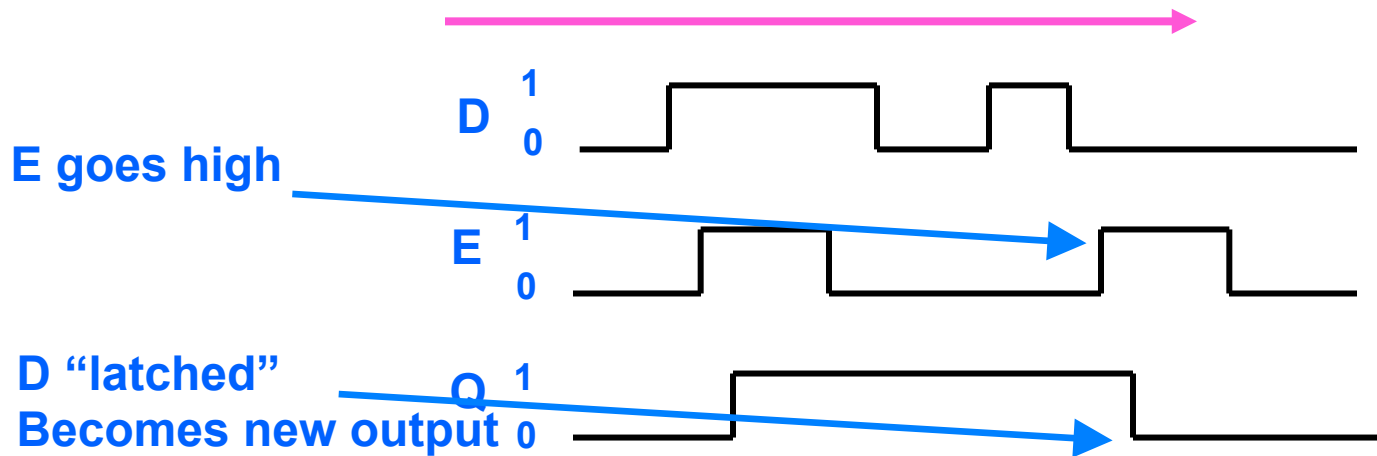

Data Latch (D Latch)

 

D	E	Q
0	1	0
1	1	1
-	0	Q

 


Logic Takes Time

- Logic takes time:
 - Gate delays: delay to switch each gate
 - Wire delays: delay for signal to travel down wire
 - Fan out: related to capacitance
- Need to make sure that signals timing is right
 - Don't want to have races or whacky conditions..

Clocks

 
- Processors have a clock:
 - Alternates 0 1 0 1
 - Latch -> logic -> latch in one clock cycle



 - 3.4 GHz processor = 3.4 Billion clock cycles/sec


Strawman: Level Triggered

- First thoughts: Level Triggered
 - Latch enabled when clock is high
 - Hold value when clock is low




Strawman: Level Triggered

 - How we'd like this to work
 - Clock is low, all values stable




Strawman: Level Triggered

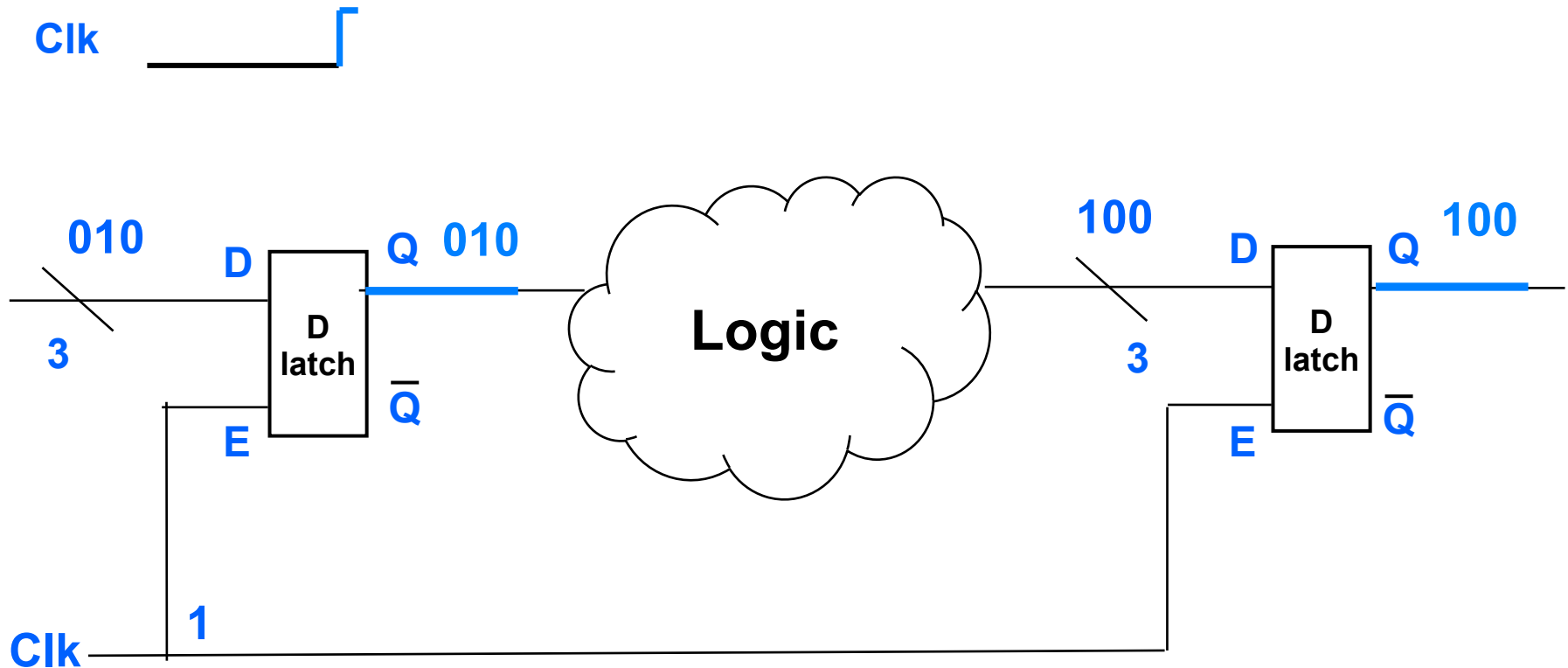- How we'd like this to work
 - Clock goes high, latches capture and xmit new val




Strawman: Level Triggered

 - How we'd like this to work
 - Signals work their way through logic w/ high clk




Strawman: Level Triggered

 - How we'd like this to work
 - Clock goes low before signals reach next latch




Strawman: Level Triggered

 - How we'd like this to work
 - Clock goes low before signals reach next latch




Strawman: Level Triggered

 - How we'd like this to work
 - Everything stable before clk goes high




Strawman: Level Triggered

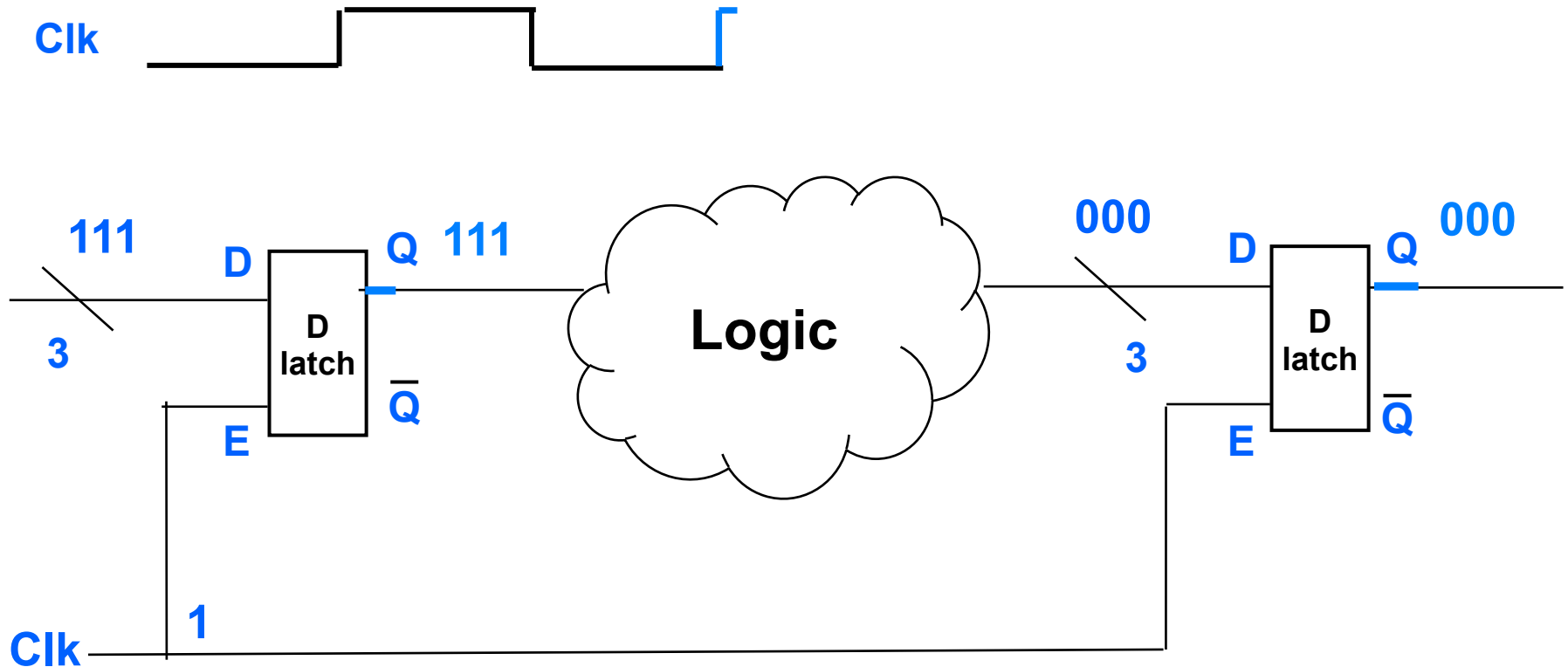- How we'd like this to work
 - Clk goes high again, repeat




Strawman: Level Triggered

 - Problem: What if signal reaches latch too early?
 - I.e., while clk is still high




Strawman: Level Triggered

 - Problem: What if signal reaches latch too early?
 - Signal goes right through latch, into next stage..



That would be bad...

 
- Getting into a stage too early is bad
 - Something else is going on there: corrupted
 - Also may be a loop with one latch
- Consider incrementing counter
 - Too fast: increment twice? Eeep...



Edge Triggered


- Instead of level triggered
 - Latch a new value at a level (high or low)
- We use edge triggered
 - Latch a value at an edge (rising or falling)

Rising Edges

 


Falling Edges

D Flip-Flop

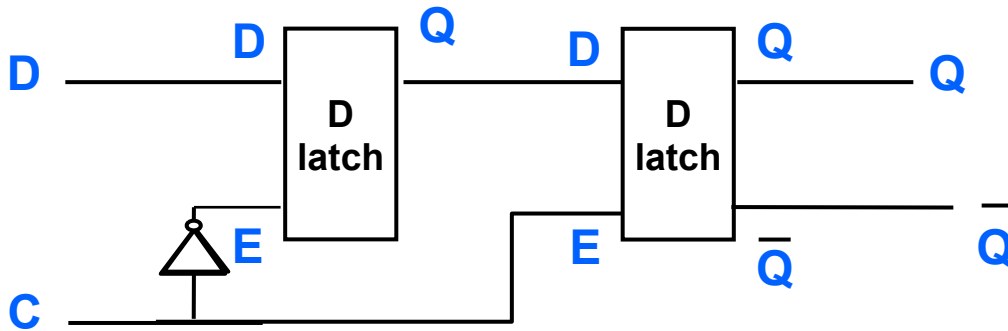


- Rising edge triggered D Flip-flop
 - Two D Latches w/ Opposite clking of enables

D Flip-Flop

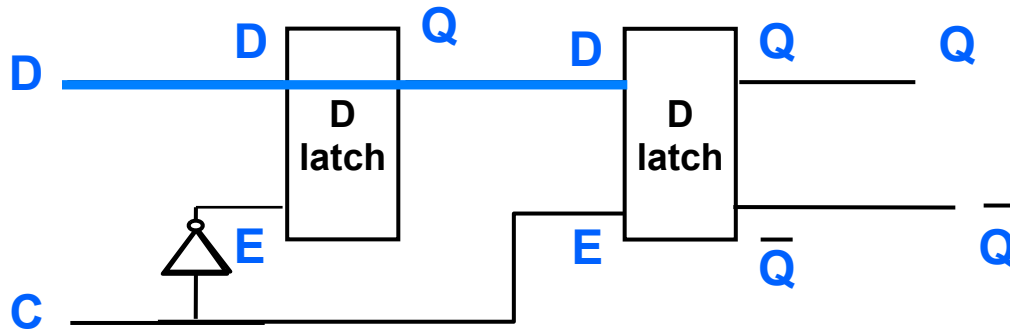


- Rising edge triggered D Flip-flop
 - Two D Latches w/ Opposite clking of enables
 - On Low Clk, first latch enabled (propagates value)
 - Second not enabled, maintains value

D Flip-Flop

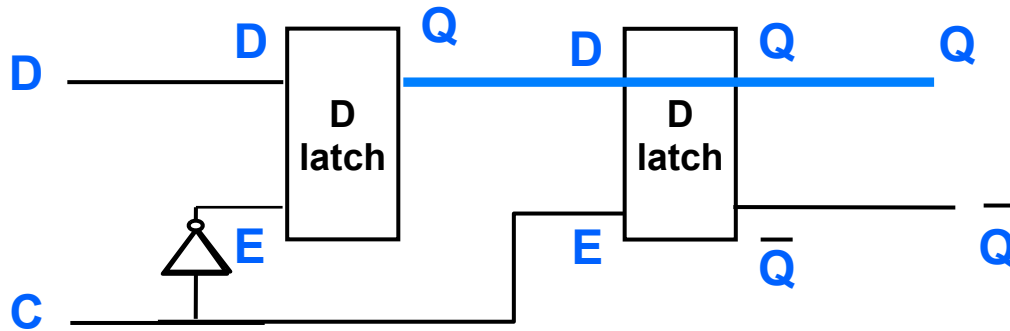

- Rising edge triggered D Flip-flop
 - Two D Latches w/ Opposite clking of enables
 - On Low Clk, first latch enabled (propagates value)
 - Second not enabled, maintains value
 - On High Clk, second latch enabled
 - First latch not enabled, maintains value

D Flip-Flop

 

- No possibility of “races” anymore
 - Even if I put 2 DFFs back-to-back...
 - By the time signal gets through 2nd latch of 1st DFF 1st latch of 2nd DFF is disabled
- Still must ensure signals reach DFF before clk rises
 - Important concern in logic design “making timing”

Making Timing




- Making timing is important in a design
 - If you don't make timing, your logic won't compute right
- Synthesis tool (Quartus) tells you what max freq
 - Running above this your logic doesn't "finish" in time

D Flip-flops (continued...)

- Could also do falling edge triggered
 - Switch which latch has NOT on clk
- D Flip-flop is ubiquitous
 - Typically people just say “latch” and mean DFF
 - Which edge: doesn't matter
 - As long as consistent in entire design
 - We'll use rising edge

D flip flops

   - Generally don't draw clk input
 - Have one global clk, assume it goes there
 - Often see $>$ as symbol meaning clk
- Maybe have explicit enable
 - Might not want to write every cycle
 - If no enable signal shown, implies always enabled




- Get output and NOT(output) for "free"

DFFs in VHDL

```
x: dffe port map (  
    clk => clk,           --the clock  
    d => someInput,       --the input is d  
    q => theOutput,       --the output is q  
    ena => en,            --the enable  
    clrn => not(rst),     --clear  
    prn => '1');         --set
```

Also, comes in "dff" with no enable

A word of advice

 

```
signal x_q : std_logic;  
signal x_d: std_logic;  
x : dfbe port map (... , d=> x_d, q=>x_q, ...);
```

- Use naming convention: x_d, x_q
- Write x_d, read x_q
- Remember new value shows up next cycle

A few words about timing

- Homework 2: VGA Controller
 - Requires certain clock frequency
 - Else won't control monitor properly
- Quartus will tell you what timing you make
 - Fmax : how fast can this be clocked
 - Tells you your worst timing paths
 - From which dff to which dff
 - Can see in schematic viewer (usually)
- Homework 2
 - Should be plenty of slack
 - But if not...


Fixing timing misses

- Typical approach: reduce logic (gate delays)
 - Better adder?
 - Rethink approach?
 - Change “don’t care” behavior?
- Fix high fanout
 - Duplicate high FO/simple logic
- Also, feel free to ask for help from me/Tas
 - Quartus’s tools to help you fix them aren’t the best

Register File

- Can store one value... How about many?
- Register File
 - In processor, holds values it computes on
 - MIPS, 32 32-bit registers
- How do we build a Register File using D Flip-Flops?
- What other components do we need?


Register File: Interface

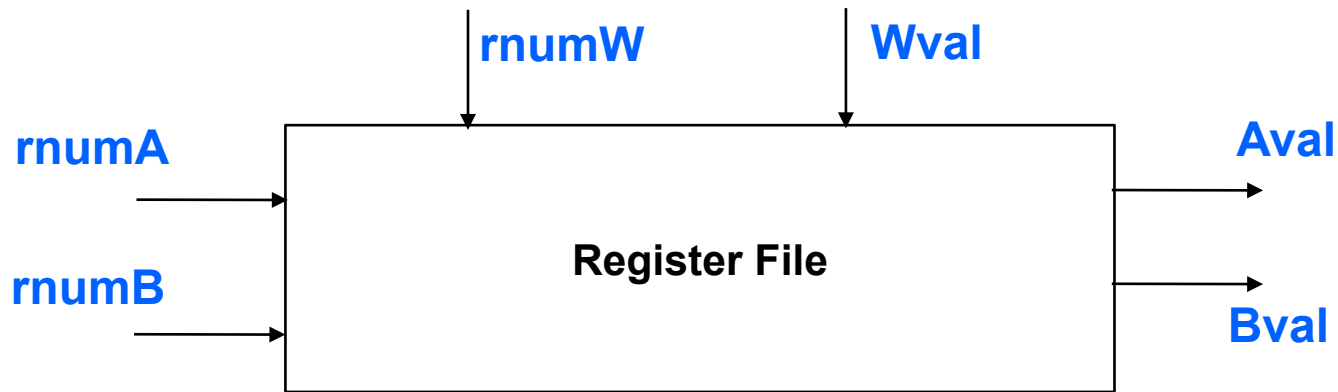

- 4 inputs
 - 3 register numbers (5 bit): 2 read, 1 write
 - 1 register write value (32 bits)
- 2 outputs
 - 2 register values (32 bits)

Register file strawman

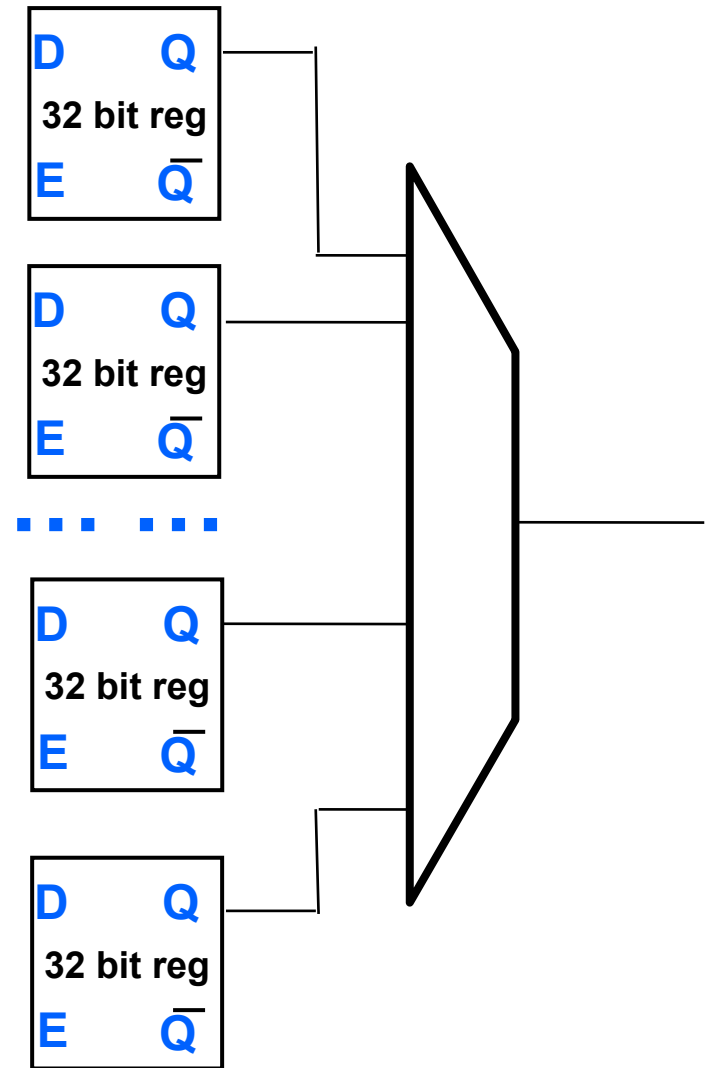- Use a mux to pick read ?
 - 32 input mux = slow
 - (other regs not pictured)




Register file strawman

- Use a mux to pick read ?

- 32 input mux = slow
- other regs not pictured


- Writing the registers

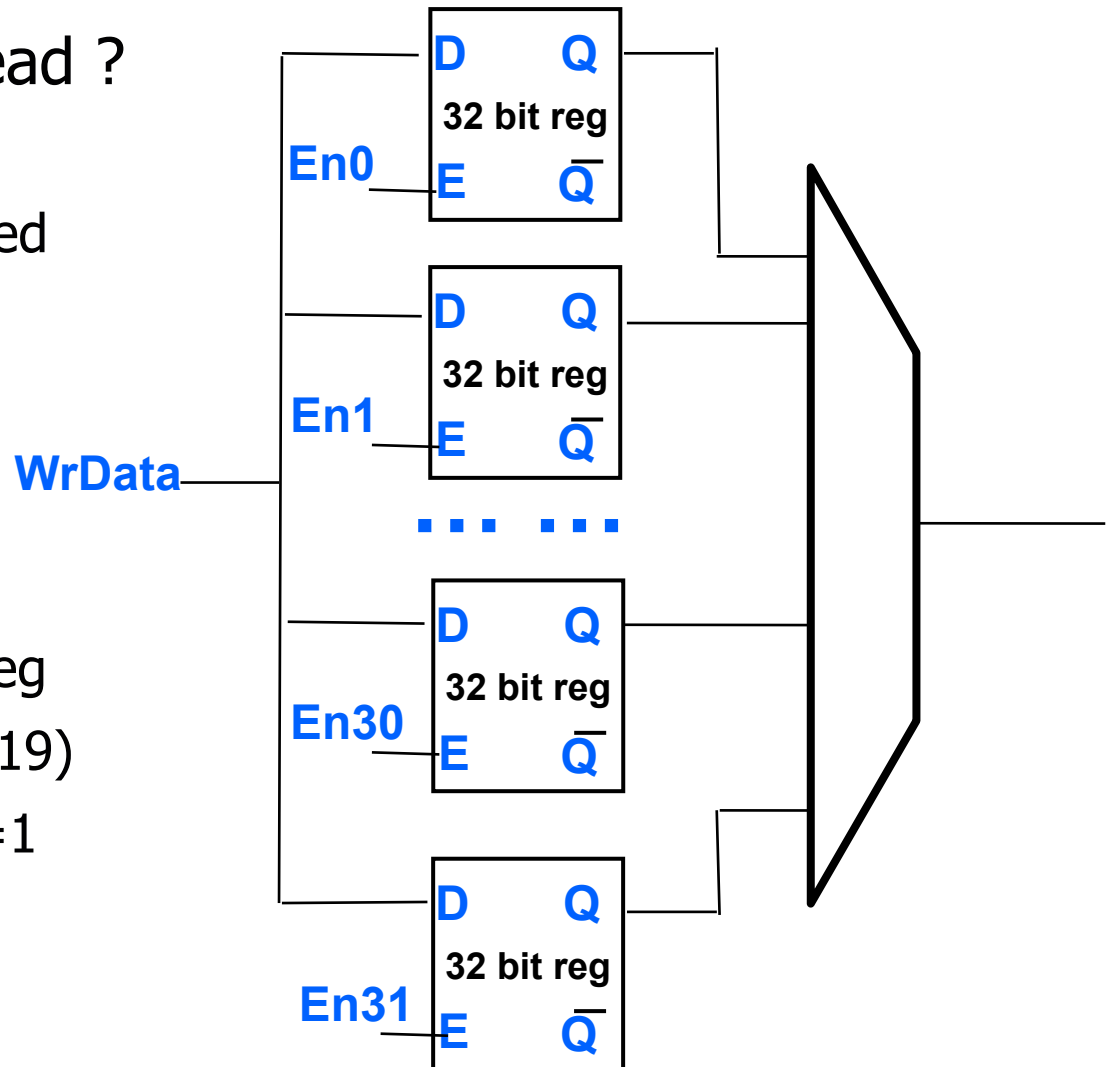- Need to pick which reg
- Have reg num (e.g., 19)
- Need to make $En_{19}=1$
 - $En_0, En_1, \dots = 0$



First: A Decoder

 - First task: convert binary number to “one hot”
 - Saw this before
 - Take register number




Register File

- Now we know how to write:
 - Use decoder to convert reg # to one hot
 - Send write data to all regs
 - Use one hot encoding of reg # to enable right reg
- Still need to fix read side
 - 32 input mux (the way we've made it) not realistic
 - To do this: expand our world from 1, 0 to 1, 0, Z

CMOS: Complementary MOS

V_{cc}

 


- 2 inputs: E and D. What does this do?
 - Write truth table for output

E	D	Output
0	0	
0	1	
1	0	
1	1	

CMOS: Complementary MOS

V_{cc}

 


- 2 inputs: E and D. What does this do?
 - Write truth table for output
 - When E = 1, straightforward

E	D	Output
0	0	
0	1	
1	0	1
1	1	0

CMOS: Complementary MOS

V_{cc}

 


- 2 inputs: E and D. What does this do?
 - Write truth table for output
 - When $E = 1$, straightforward
 - When $E = 0$, no connection: Z

E	D	Output
0	0	Z
0	1	Z
1	0	1
1	1	0

High Impedance: Z

 - Z = High Impedance
 - No path to power or ground
 - "Gate" does not produce a 1 or a 0
- Previous slide: **tri-state** inverter
 - More commonly drawn: tri-state buffer
 - E = enable, D = data




D	E	Out
0	1	0
1	1	1
X	0	Z

Don't' care

Remember this rule?

 - Remember I told you not to connect two outputs?




- If one gate tries to drive a 1 and the other drives a 0
 - One pumps water in.. The other sucks it out
 - Except its electric charge, not water
 - “Short circuit”—lots of current -> lots of heat

We've had this rule one day...

**Its ok to connect multiple outputs together
Under one circumstance (*):**

 
All but one must be outputting Z at any time



(*) Disclaimer: there are other circumstances... but not doing them now

Mux, implemented with tri-states

 - We can build effectively a mux from tri-states
 - Much more efficient for large #s of inputs (e.g., 32)



Ports

- What we just saw: read port
 - Ability to do one read / clock cycle
 - Originally said want 2 reads: read 2 src registers /insn
 - Maybe even more if we do many insns at once
- This design: can just put replicate
 - Another decoder
 - Another set of tri-states
 - Another output bus (wire connecting the tri-states)
- Earlier: write port
 - Ability to do one write/cycle
 - Could add more: need muxes to pick wr values

Minor Detail

- FYI: This is not how a register file is implemented
 - (Though it is how other things are implemented)
 - Actually done with SRAM
 - We'll see how those work soon

Summary

Can layout logic to compute things

Add, subtract,...

Now can store things

D flip-flops

Registers

Also understand clocks